

Ship Of Theseus: compatible, interchangeable amp modules

by Mark Johnson

[rev 2022 March 02]


This project extends the limited-edition Nelson Pass / diyAudio "VFET" kits, by introducing several new circuit modules which are compatible and interchangeable with the modules in the original kit. At this writing, the Ship Of Theseus includes seven new Front End cards, a new PSU filter card (with turnoff thump suppression), and a new output stage card which uses active-production MOSFETs instead of rare and obsolete VFET transistors.

Owners of an original VFET kit can experiment with different Front Ends to customize their amplifier, and tailor it to their own sonic preference. They also can drop in the new PSU filter card, to enjoy its turnon/turnoff thump reduction and improved 120 Hz filtering.

Builders without an original VFET kit will need Front End cards, a PSU filter card, and output stage cards. The Ship Of Theseus portfolio of choices, provides several possibilities.

MOSFET Output Stage

A Pchannel MOSFET (Q6) drives the output, operating as a source follower in Class A. 1.6 amperes of constant current bias are provided by Q5 and the IC shunt reference U2. Q2 and Q3 drive the substantial gate capacitance of Q6. Because Q6 is an "enhancement mode" PMOSFET, its source voltage is always higher than its gate voltage. To increase the available output swing on negative peaks, the gate of Q6 is fed by a special power supply module (U1) that provides negative five volts (circuit node "VNEG"). Variable resistor RV1 adjusts the quiescent voltage on the source pin of Q6. It should be set to half of the supply voltage.

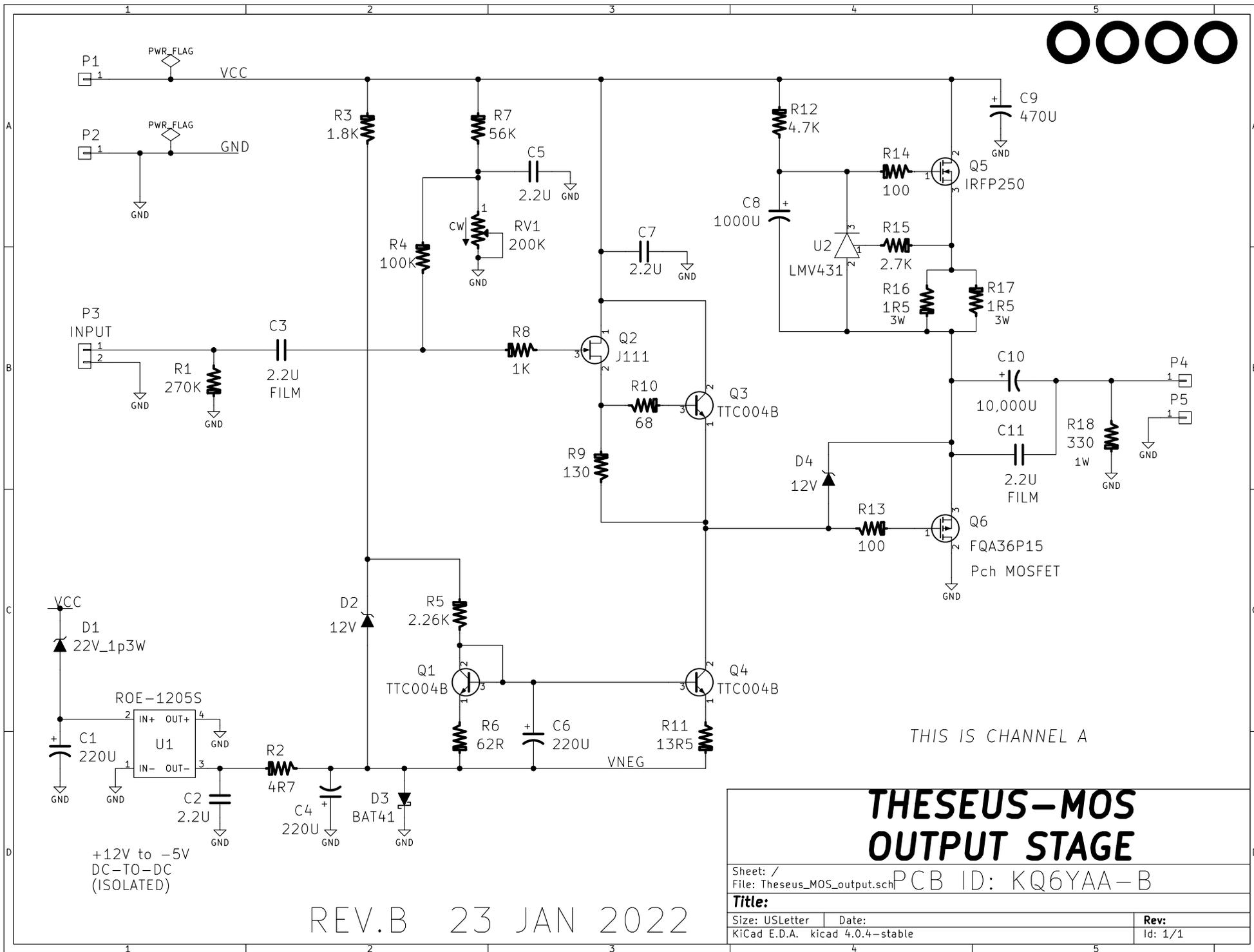


+12V to -5V
DC-TO-DC
(ISOLATED)

REV.B 23 JAN 2022

THESEUS-MOS OUTPUT STAGE

Sheet: /		File: Theseus_MOS_output.sch		PCB ID: KQ6YAA-B	
Title:		Size: USLetter		Date:	
KiCad E.D.A.		kicad 4.0.4-stable		Rev:	
				Id: 1/1	

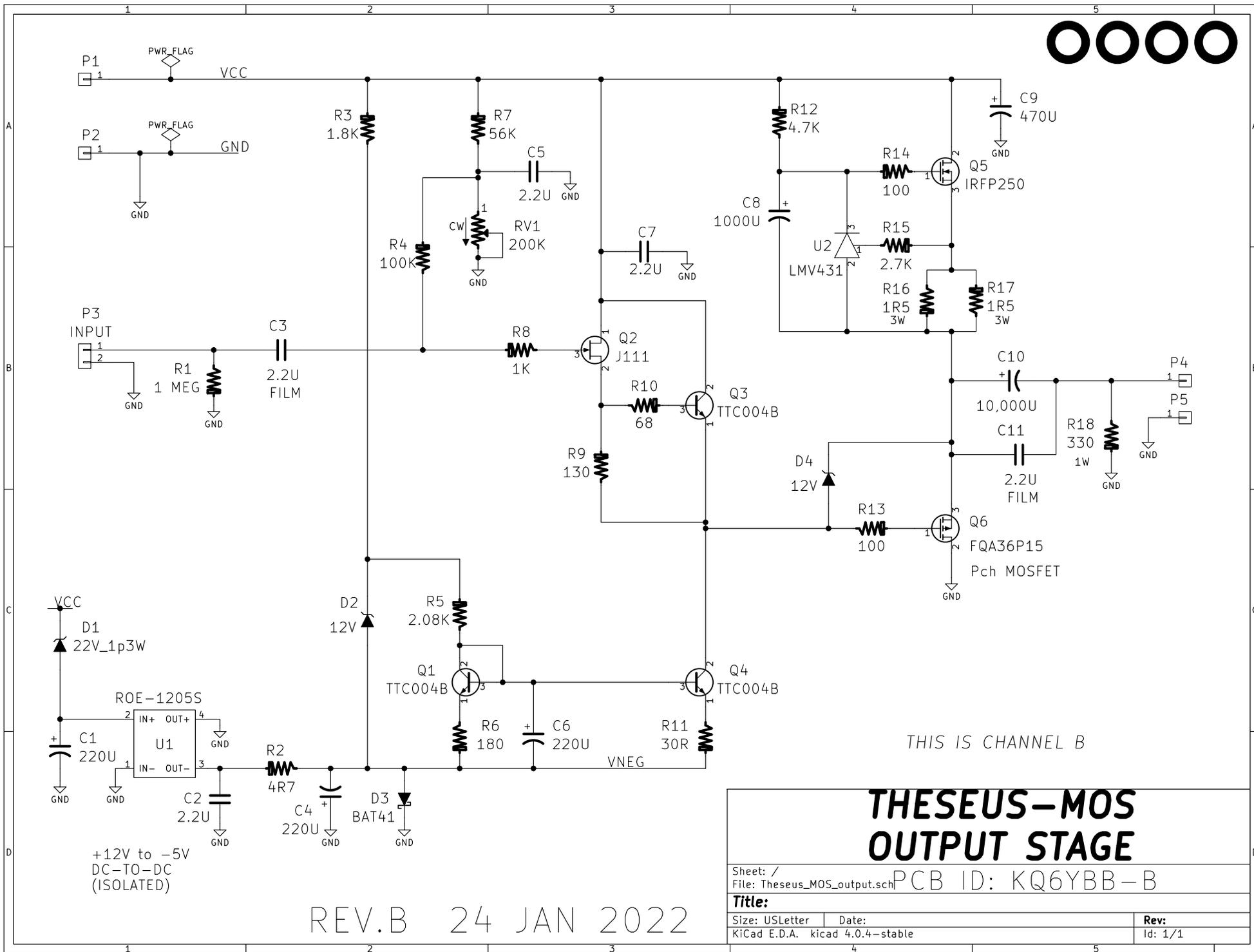

THIS IS CHANNEL B

THESEUS-MOS OUTPUT STAGE

Sheet: /
File: Theseus_MOS_output.sch PCB ID: KQ6YBB-B

Title:	
Size: USLetter	Date:
KiCad E.D.A. kicad 4.0.4-stable	Rev: Id: 1/1

REV.B 24 JAN 2022

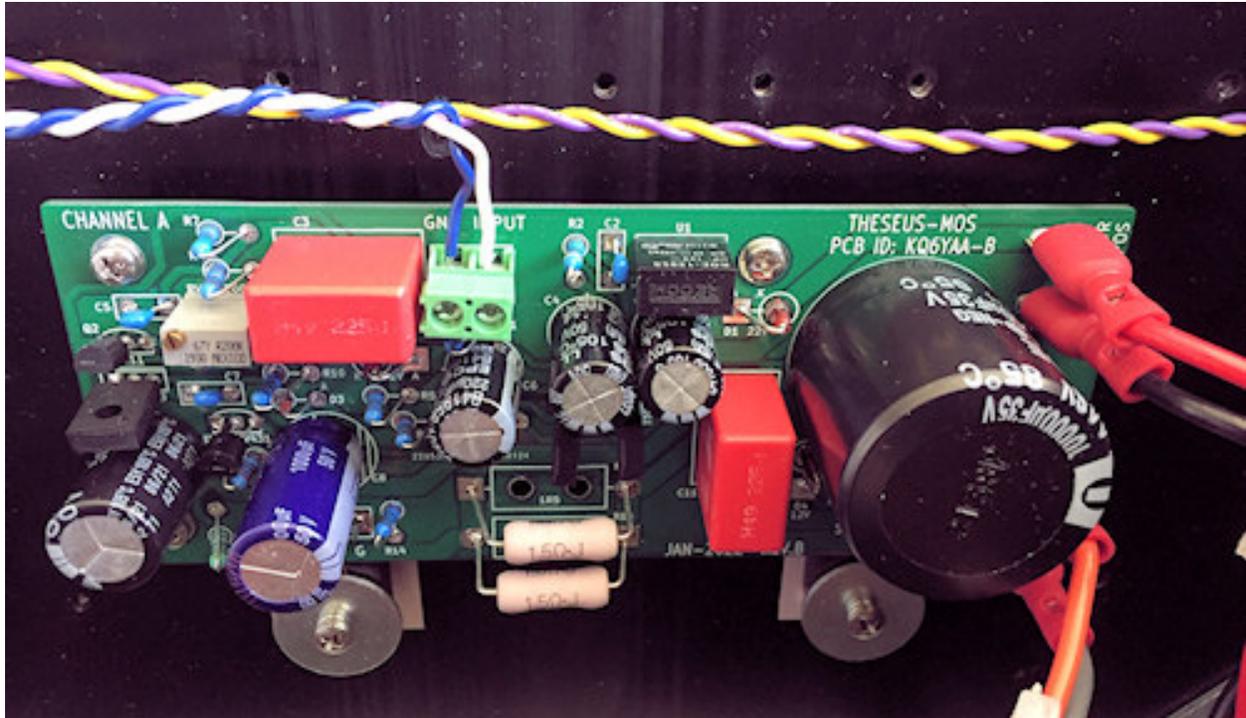


Photo 1: MOSFET output stage card. FastOn blade connectors at right

Its circuit topology closely follows the original Pchannel VFET circuit design, which had a P-type VFET follower and a 1.6 amp constant current load, provided by an IRFP250.

PSU Filter Card

Two different PSU filter cards were provided with the original VFET kits from the diyAudio Store. One card (containing an LC filter) came with the Pchannel VFET kits, and another card (containing an RC filter and a thump suppression relay) came with the Nchannel VFET kits. To remain backward compatible with both types of VFET output cards, this new Ship Of Theseus filter contains both an LC filter (L1-C1) and an RC filter (R1-C3). Ferrite beads were added, for additional high frequency noise filtering.


A more elaborate circuit for thump prevention (2nd schematic page) was included, giving user-selectable muting time at turn on, and near-instantaneous muting at turn off.

Ferrite Bead is Laird
28C0236-0EW-10

Inductor is Bourns
RL622-100K-RC

Capacitors are LS=7.5
Dia=16 Panasonic FR/FM
EEU-FM1H102B

Relay is 24V coil
29mm X 12.7mm

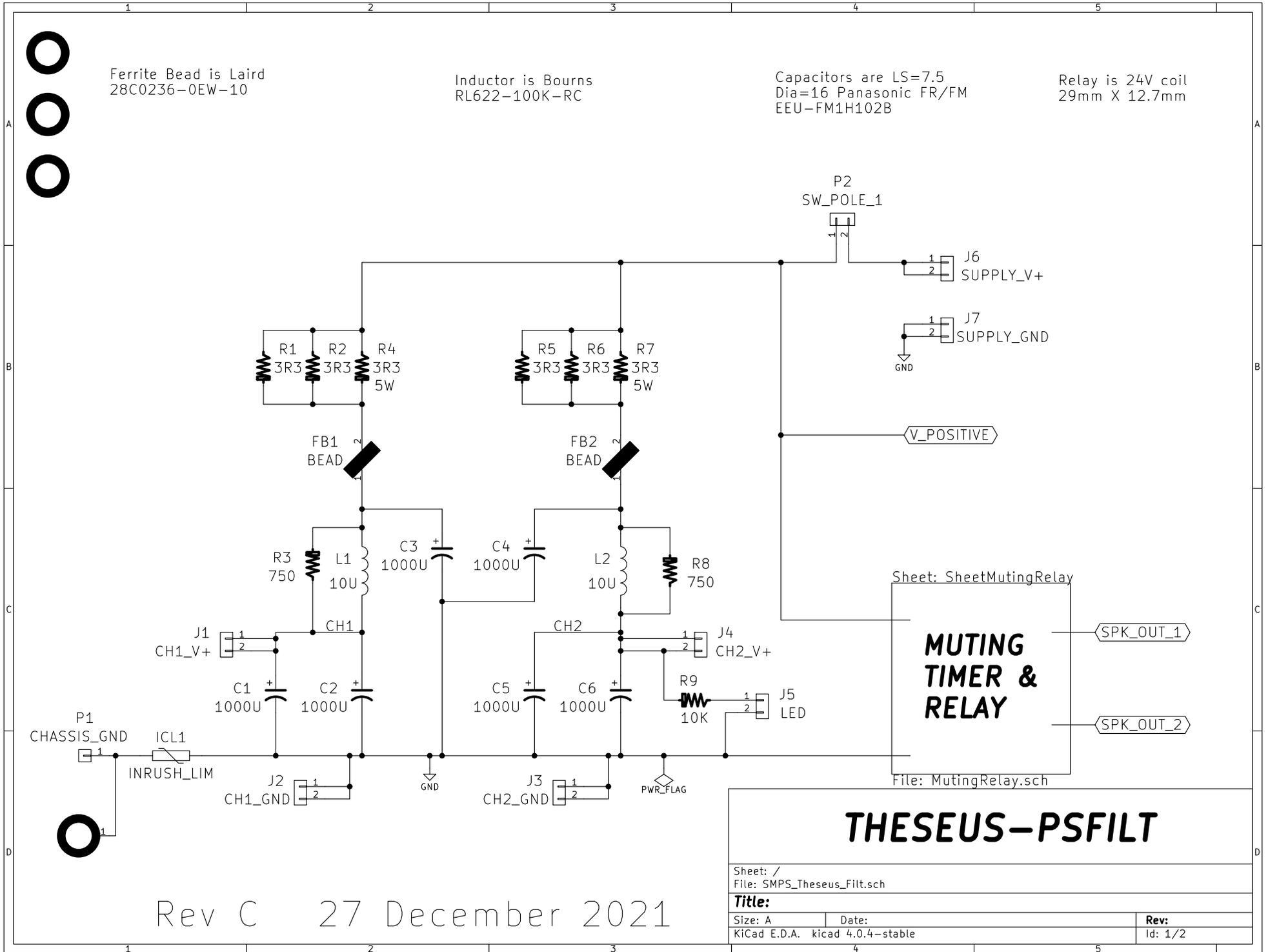

Sheet: SheetMutingRelay


**MUTING
TIMER &
RELAY**

File: MutingRelay.sch

THESEUS-PSFILT

Sheet: /		File: SMPS_Theseus_Filt.sch	
Title:			
Size: A	Date:	Rev:	
KiCad E.D.A.	kicad 4.0.4-stable	Id: 1/2	

Rev C 27 December 2021

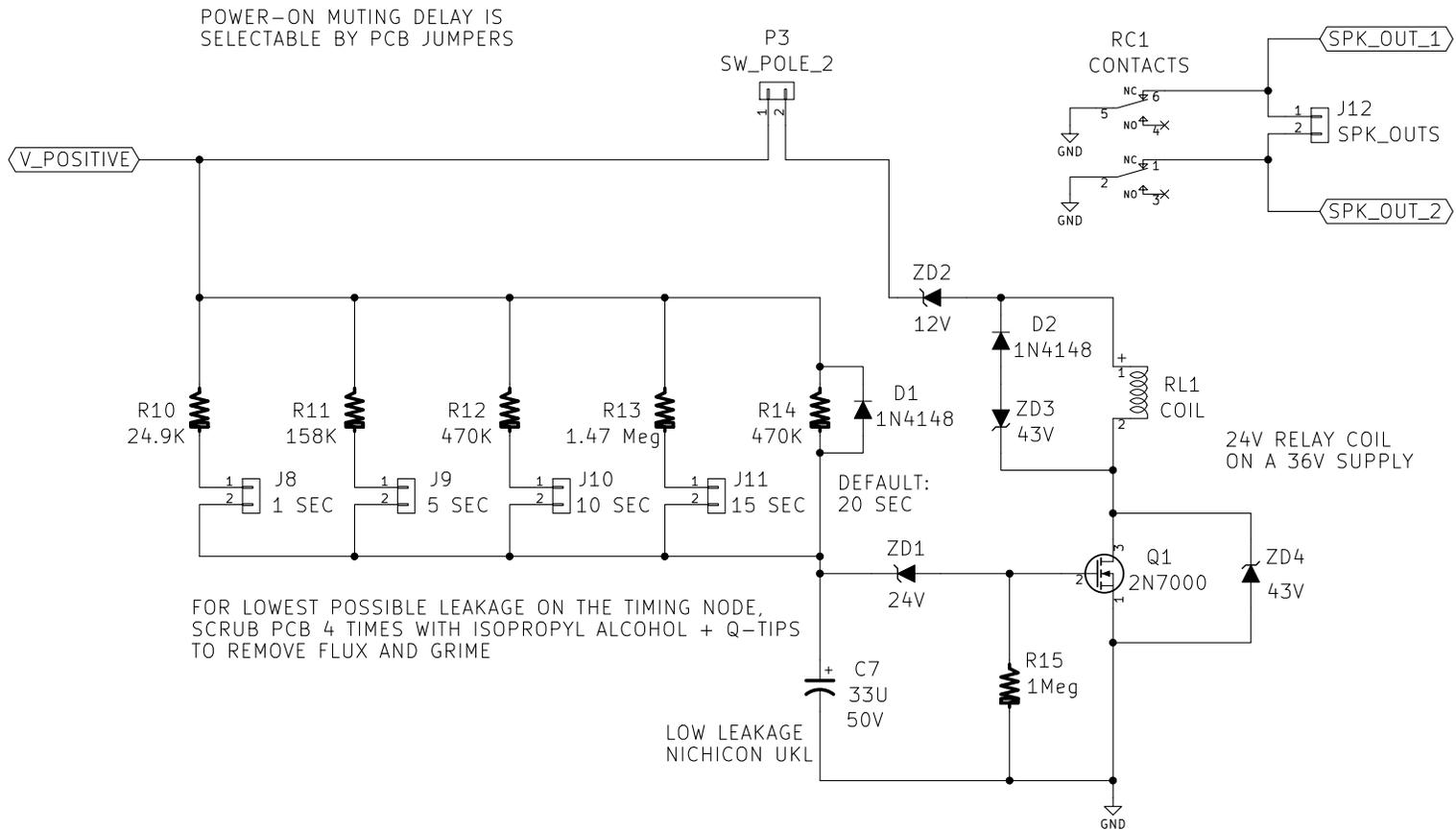

MUTING RELAY FOR THESEUS-PSFILT

Sheet: /SheetMutingRelay/
File: MutingRelay.sch

Title:

Size: A4

Date:

KiCad E.D.A. kicad 4.0.4-stable

Rev:

Id: 2/2

Rev C 27 December 2021

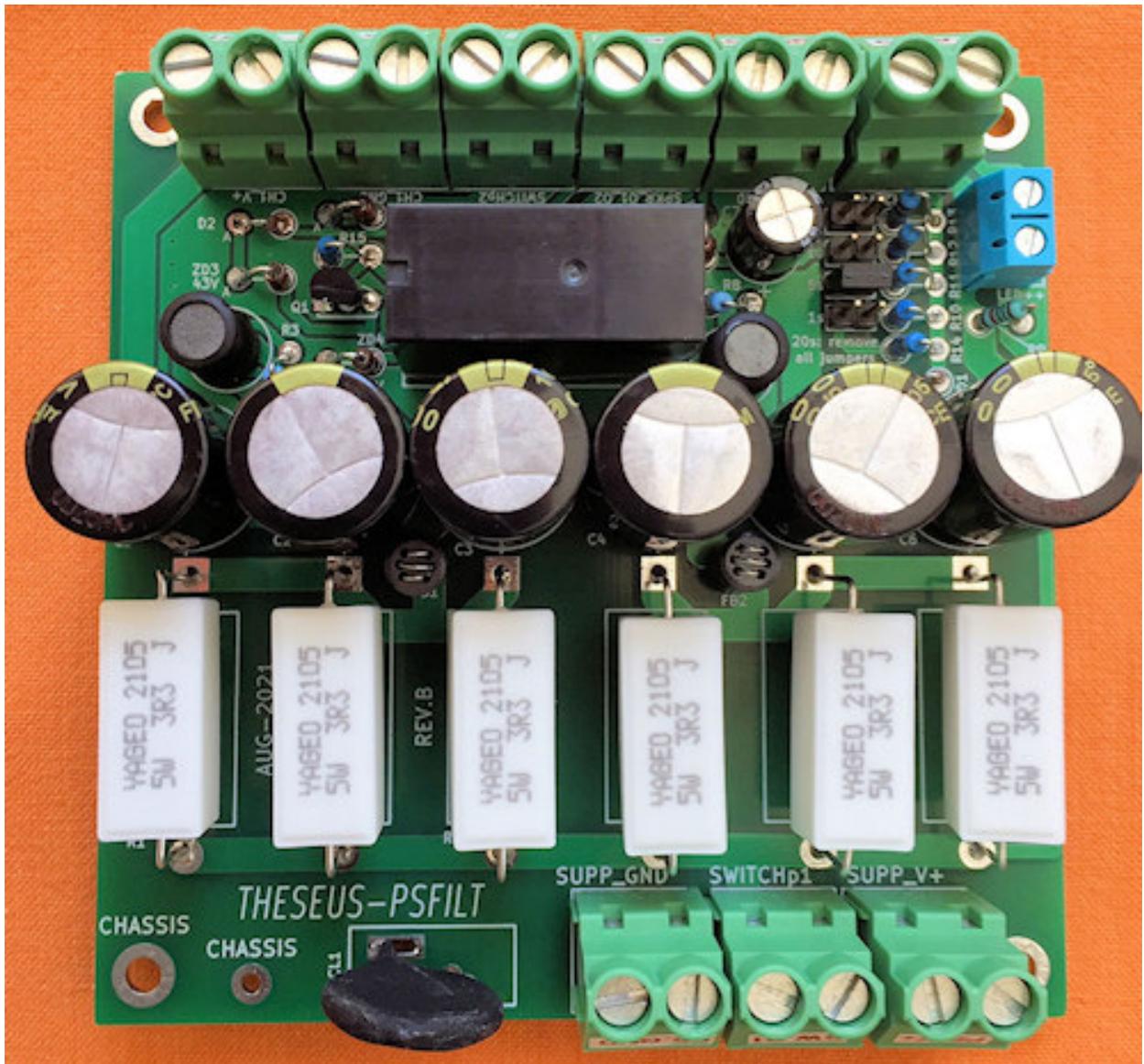


Photo 2: PSU filter card. Muting relay at top center

Front End cards

Ship Of Theseus provides seven new front ends, in addition to Nelson Pass's original card (Toshiba JFETs) shipped with the diyAudio kits, and in addition to the Scourge, Bulwark, Marauder, and Dreadnought cards sold by the diyAudio Store. These new cards are named for American warships. A brief summary of their features is presented here; more thorough discussions follow.

Nimitz is a customizable Front End which accepts M2x daughter cards. Builders can bolt whichever M2x card they wish into Nimitz, and that becomes the Front End for a VFET or Theseus amplifier.

Missouri is a Front End that accepts balanced inputs. It uses the highly regarded THAT-1200 differential receiver IC for maximum CMRR

Bon Homme Richard is a high performance opamp (AD797), plus a discrete JFET input stage, fed by a shunt-mode voltage regulator for maximum PSRR

Kitty Hawk is a transconductance (current output) amplifier, which uses a Rush Cascode input stage: PNP follower + NJFET common gate.

Lexington is a folded cascode discrete opamp, using a self-generated high voltage supply ("JBOOST2") and no Edecor transformer. The boost circuit includes an isolated DC-to-DC converter module plus extensive filtering.

Hornet is a discrete opamp whose unusual all-JFET output stage has no degeneration resistors. The supply filter is cascoded, each of the two constant current sources are cascoded, and the input is a Rush Cascode.

Pequod was Captain Ahab's whaling ship in "Moby Dick." Although not a warship, it was American. The Pequod Front End is a simple opamp follower with few parts and relatively modest parts cost. It accepts either dual opamps (e.g. LM4562) or single opamps (e.g. LT1122) and the two opamp sockets are surrounded by blank empty zones, making it easier to fit discrete opamp modules such as Sparkos or Burson, if desired.

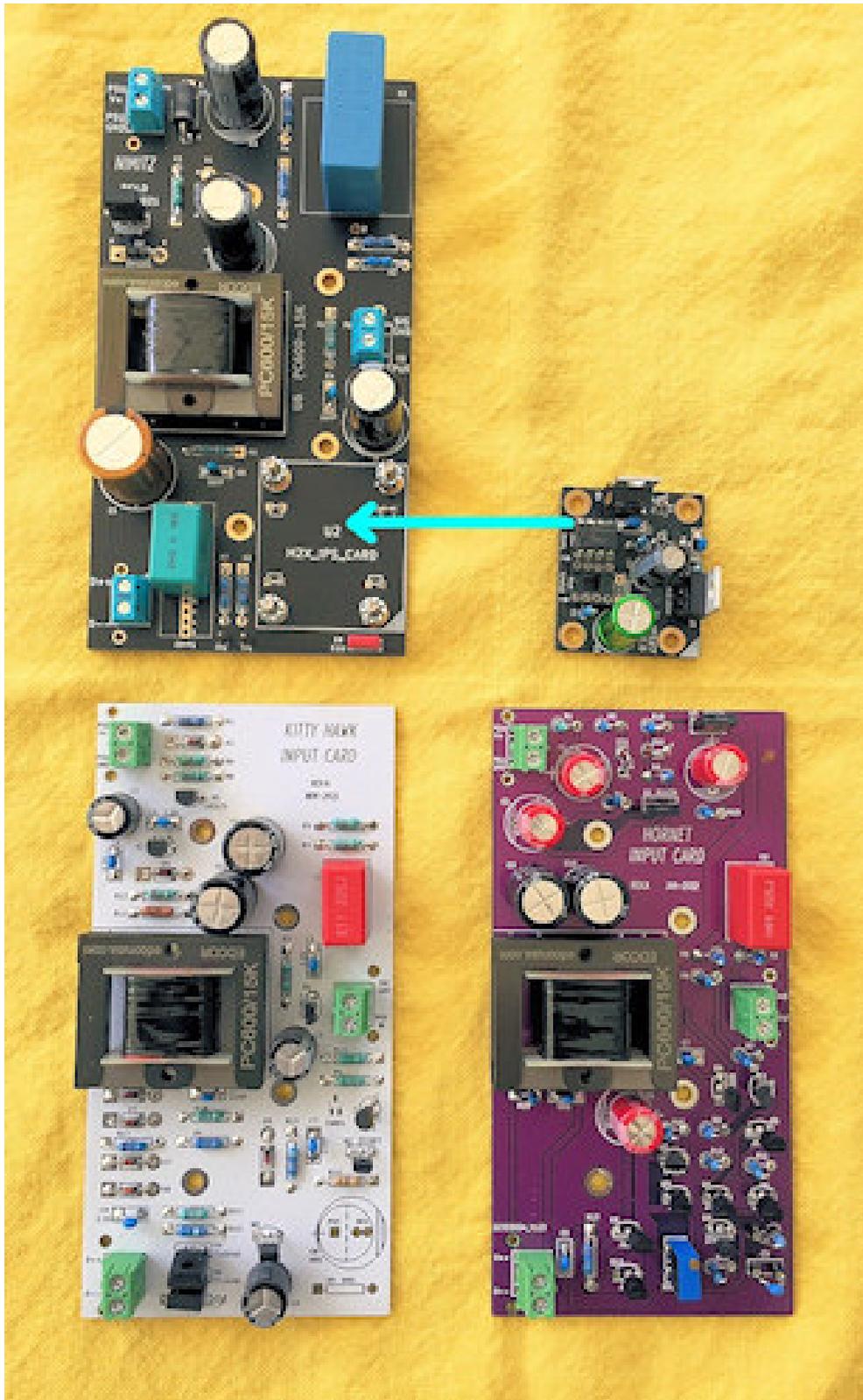


Photo 3: Nimitz, daughter, Hornet, Kitty Hawk

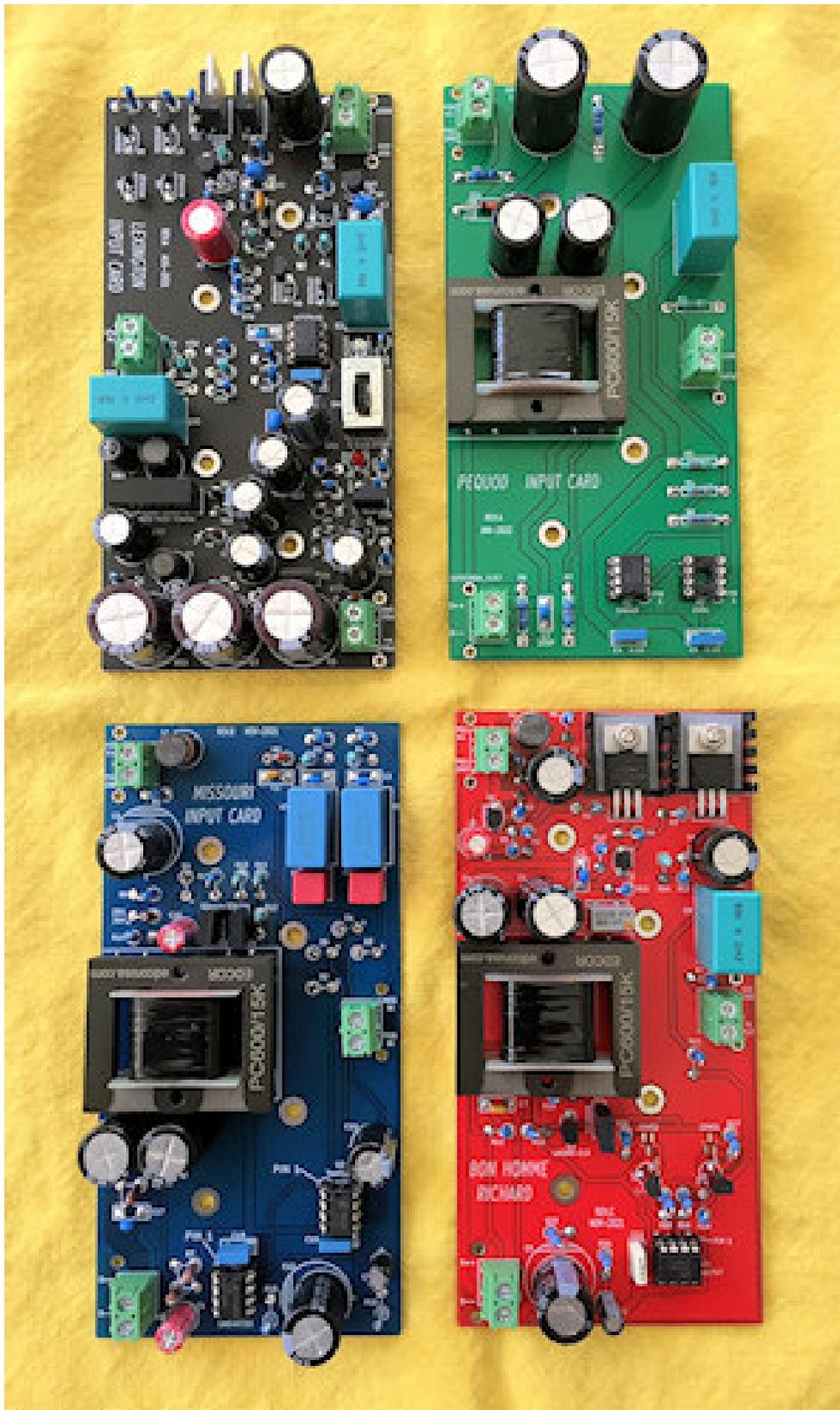


Photo 4: Lexington, Piquod, Bon Homme Richard, Missouri


Nimitz Front End

Theseus / VFET builders who already own an M2x amplifier, probably have a favorite M2x input daughter card. Nimitz allows them to try out that M2x input card in the new amplifier. Maybe lightning strikes twice (?).

Schottky diode D3 attempts to protect the daughter card, and indeed all of Nimitz, if the supply is accidentally connected backwards. It would be a shame to destroy the Front End because of such a mistake, but a *crying shame* to also destroy a Norwood or a Cedarburg card in the process.

Capacitance multiplier Q1-R3-C3 attenuates any 100 or 120 Hz ripple that might be present on the DC supply, by about 35-40 dB.

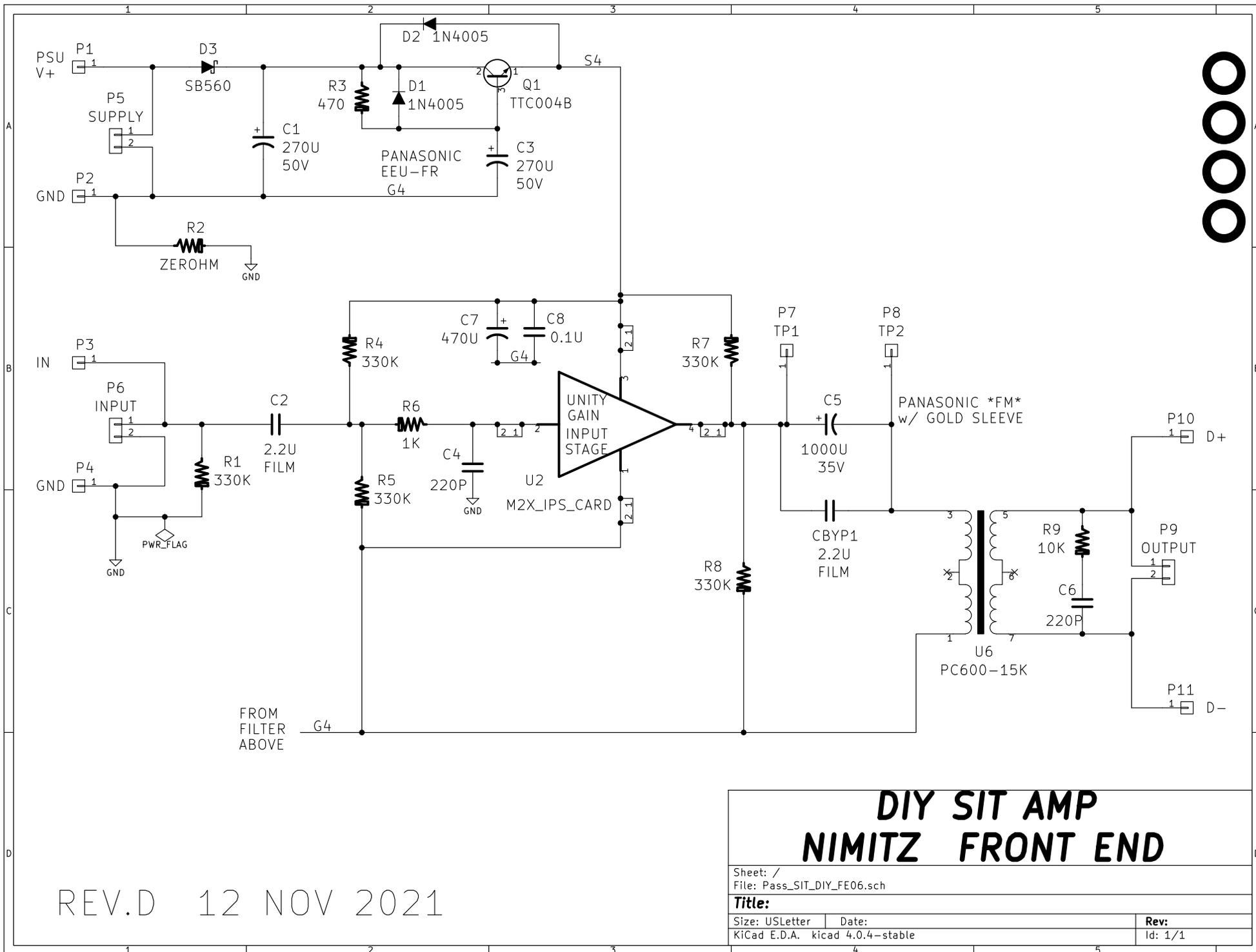Nimitz's electrolytic output capacitor (C5) is bypassed by a polypropylene film capacitor (CBYP1), in an attempt to be calm nervous audiophiles. Test points TP1 and TP2 are provided, allowing courageous builders to perform various kinds of invasive and potentially dangerous surgery upon the circuit. An opportunity for creative ingenuity.



REV.D 12 NOV 2021


Missouri Front End

Only a small percentage of First Watt / diyAudio Store amplifiers, have the ability to accept XLR or balanced inputs, a limitation which some builders consider a deal breaker. Missouri is an attempt to correct that, for the VFET and Theseus families of amplifiers.


A balanced input signal is provided at input connector P2 (XLR pin 1 is connected to the amplifier chassis). This is applied to a professional audio IC called "THAT-1200" whose patented design maximizes common mode rejection. Compare the Missouri schematic to the THAT Corp datasheets and application notes; you'll discover that Missouri carefully implements all of THAT Corp's recommendations.

R7-R8-C4 generate a mid supply bias voltage, which opamp U1A buffers and drives with very low impedance, into pin 1 ("REF_IN") of the THAT chip. Then U1B, whose output current specification is quite significant (23 mA into 600 ohm load), drives the Edcor transformer primary.

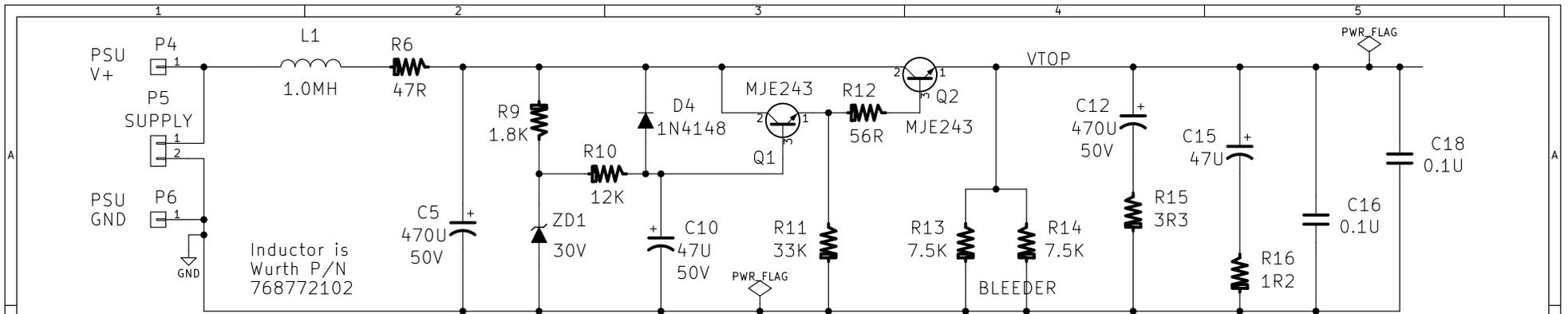Missouri includes high frequency noise filtering (L1-R6-C5), and also a darlington capacitance multiplier (R10-C10-Q1-Q2) for ripple attenuation at low frequencies.



POWER SUPPLY FILTERING

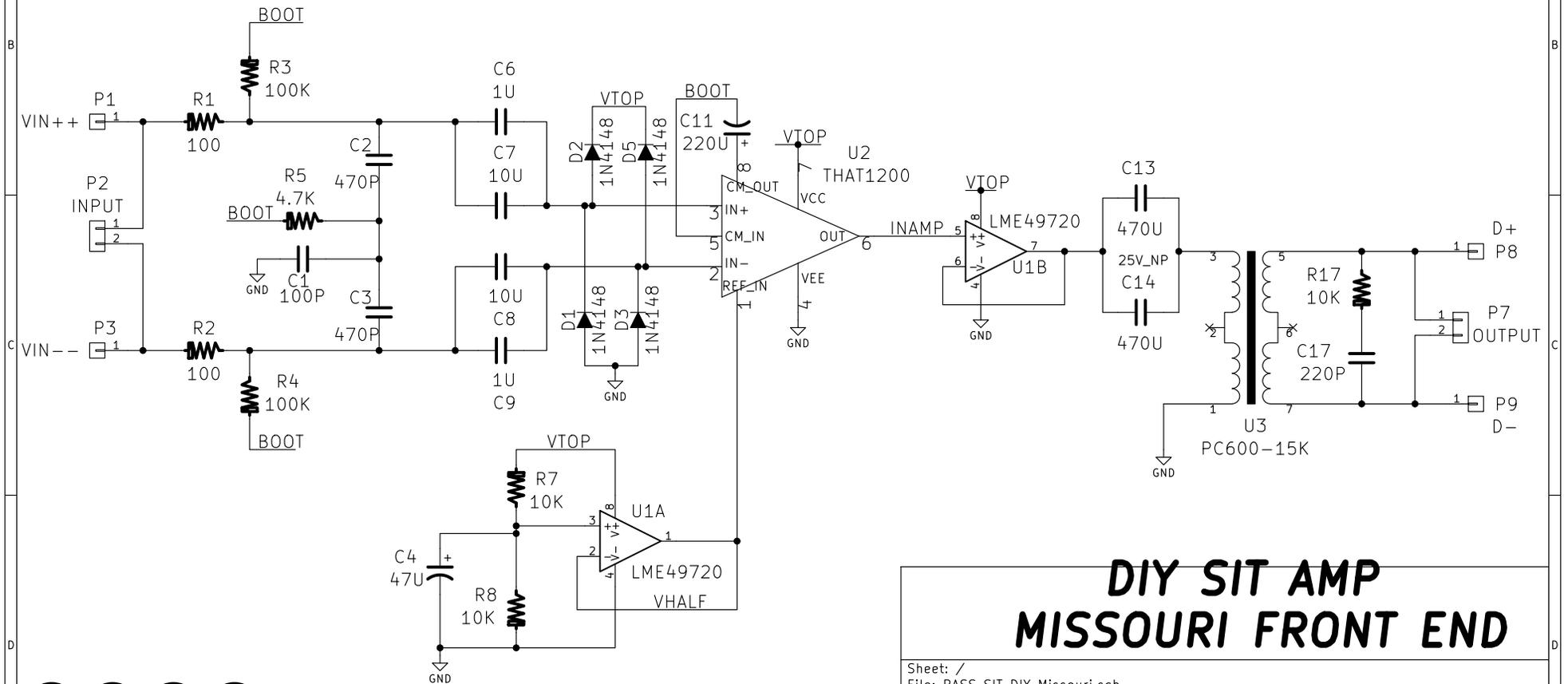

**DIY SIT AMP
MISSOURI FRONT END**



REV.B 11 NOV 2021

Sheet: /		File: PASS_SIT_DIY_Missouri.sch	
Title:			
Size: USLetter	Date:	Rev:	
KiCad E.D.A.	kicad 4.0.4-stable	Id: 1/1	

Bon Homme Richard Front End

This Front End card is a shining example of the audiophile mantra “anything worth doing is worth over-doing.” BHR starts with a wicked good (expensive!) opamp, adds wicked good power supply regulation, and finishes up with painstakingly hand-matched components.

The resistor matching exercise was discussed / beaten to death during Nov 2021, in a diyAudio thread entitled “Resistor matching error starting with six 1% resistors”. I will attempt to link that thread here:

<https://www.diyaudio.com/community/threads/resistor-matching-error-starting-with-six-1-resistors.379344/>


The power supply section of BHR includes a passive noise filter (L1-R1-C1), followed by a shunt voltage regulator. The regulator consists of a constant current source (Q1-M1), a darlington power transistor as the shunt (Q2), and an error amplifier (U1) connected in a negative feedback loop around Q2. Circuit performance, PSRR, is set by a simple impedance divider, whose upper impedance is the output impedance of the CCS, and whose lower impedance is the output impedance of the shunt device (including NFB). The former is very large and the latter is very small, so the division ratio is extremely small, and the PSRR is a very large negative number of dBs.

The wicked good opamp, AD797, is notoriously temperamental when operated at unity gain, as is done in Front End cards using an Ecor step up transformer. BHR’s solution is to attenuate the input by a factor of 4X, then operate the AD797 at a gain of 4. Presto, stability and adequate phase margin are preserved. {math note: $470/120 = 3.917$, in fact}


The attenuator (schematic page two) is a differential-in, differential-out discrete circuit consisting of two JFETs and four resistors. Its PCB layout accepts either surface mount JFETs or thru-hole JFETS; the builder can choose either.



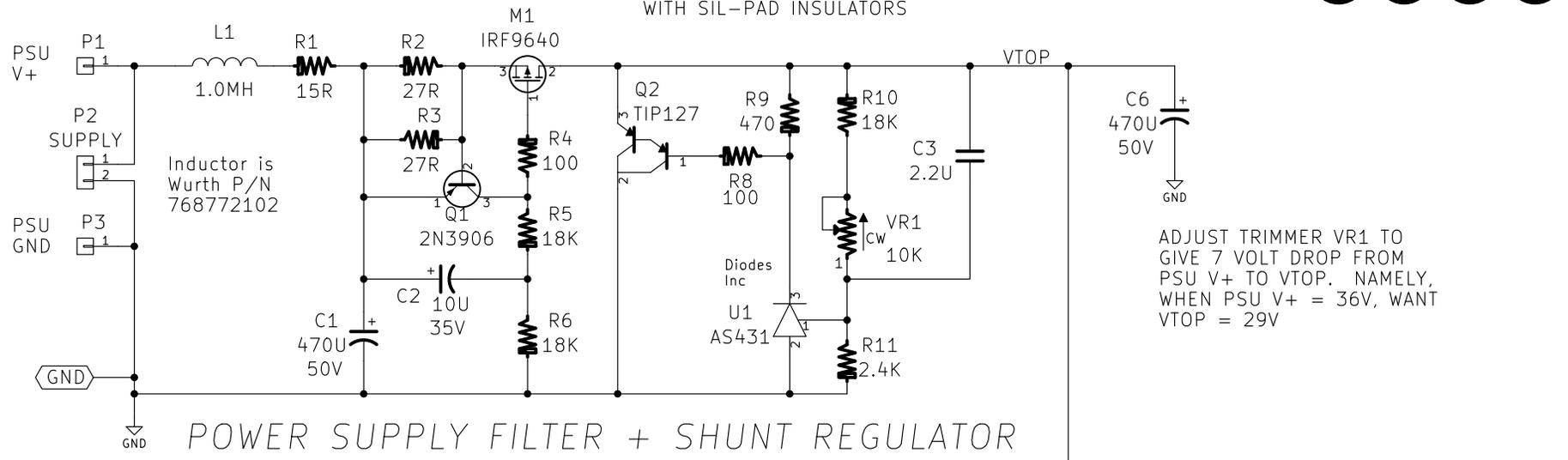M1 AND Q2 ARE MOUNTED ON AAVID 5073 HEAT SINKS WITH SIL-PAD INSULATORS



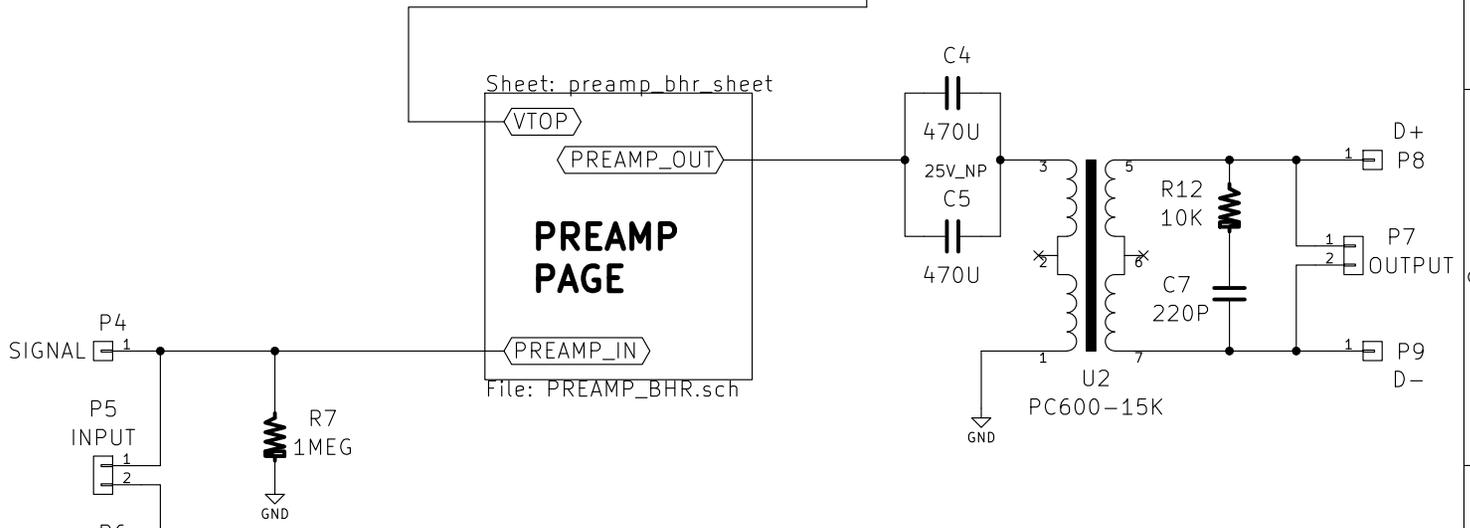M1 REQUIREMENTS:
 Pch MOS IN TO-220
 PINOUT G-D-S
 VDSmax > 50V
 IDSmax > 3A
 POWERmax > 25W
 LOTS OF OTHER PART #s WILL WORK FINE




REV.C 09 NOV 2021

DIY SIT AMP FRONT END BON HOMME RICHARD

Sheet: /		File: PASS_SIT_DIY_BonHomme.sch	
Title:			
Size: USLetter	Date:	Rev:	
KiCad E.D.A.	kicad 4.0.4-stable	Id: 1/2	

MATCH R16,R20 WITHIN 0.4%
 MATCH R17,R21 WITHIN 0.4%

REV.C 09 NOV 2021

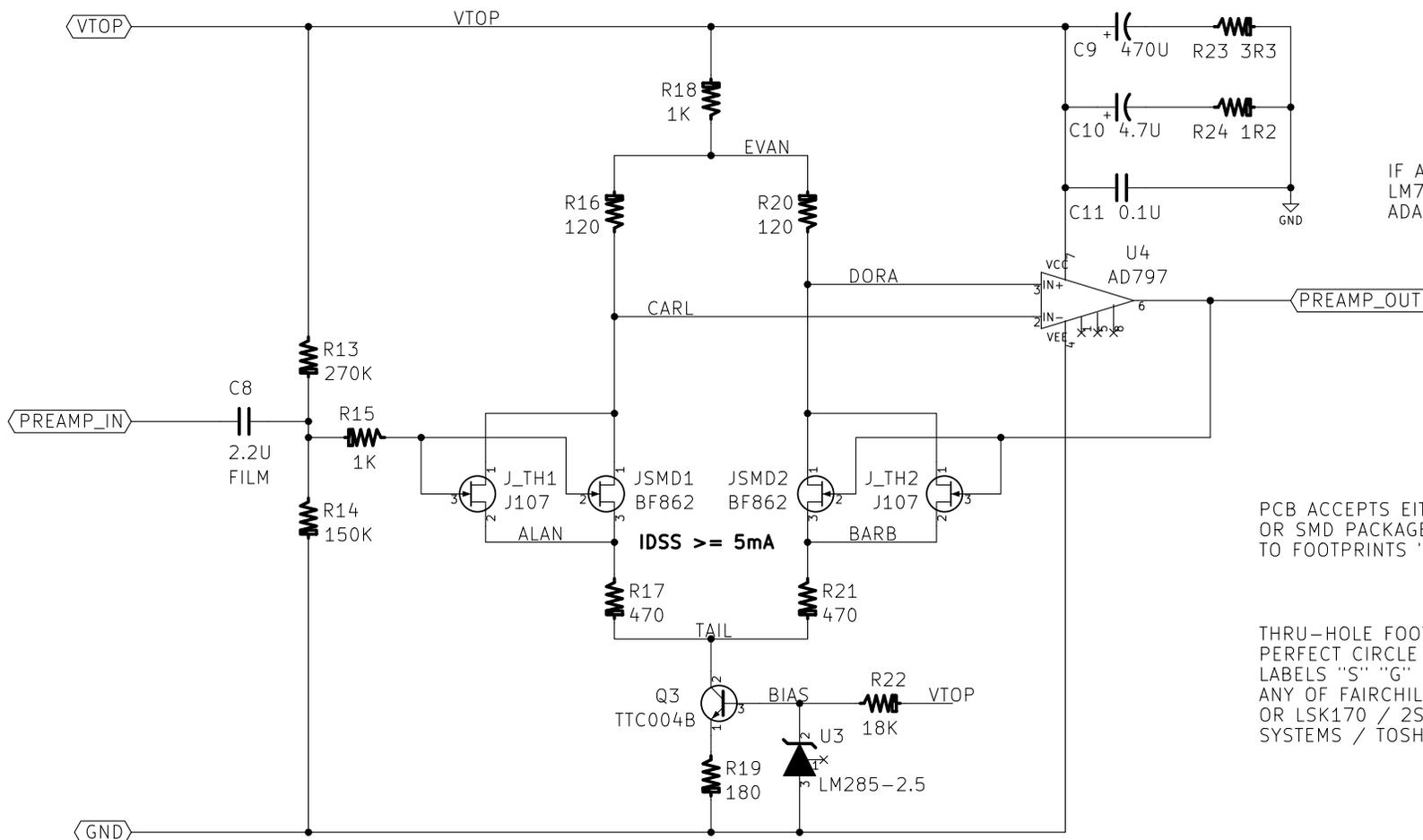

IF AD797 IS BACKORDERED:
 LM7171, LT1112, LT1363,
 ADAPTER + OPA1611 / AD825

PCB ACCEPTS EITHER THRU-HOLE
 OR SMD PACKAGED JFETS. SOLDER
 TO FOOTPRINTS "J_TH" OR "JSMD"

THRU-HOLE FOOTPRINT IS A
 PERFECT CIRCLE WITH SILK TEXT
 LABELS "S" "G" "D". CAN ACCEPT
 ANY OF FAIRCHILD J107, J112, J113
 OR LSK170 / 2SK170 FROM LINEAR
 SYSTEMS / TOSHIBA.

TO MATCH R16,R20 WITHIN 0.4% :
 BUY 6 PCS 120 OHMS 1% METAL FILM
 MEASURE ON 3.5 OR 4.5 DIGIT DMM
 CHOOSE THE PAIR WITH BEST MATCH

REPEAT WITH 6 PCS 470 OHM 1% MF

GENERAL CASE USING *N* 1% RESISTORS:
 GUARANTEED MATCH <= 2% / (N - 1)

PREAMP_BHR

Sheet: /preamp_bhr_sheet/
 File: PREAMP_BHR.sch

Title:

Size: A4

Date:

KiCad E.D.A. kicad 4.0.4-stable

Rev:

Id: 2/2

Kitty Hawk Front End

Kitty Hawk was born after ruminating upon the weaknesses of the Rush Cascode circuit. Eventually it emerged that the Rush Cascode's DC offset, drift, and temperature sensitivity are not significant, if (a) operating at low gain; and also (b) when the input and output are AC coupled. Presto! Ship Of Theseus Front Ends with Edcor transformers are low gain and AC coupled. The requirements are met.


In Kitty Hawk, a "hybrid" Rush Cascode is used, consisting of one JFET (J1) and one BJT (Q2). Together with constant current load Q1, they form the first stage of the Kitty Hawk preamp. The second stage is composed of Q3-Q4, with constant current load Q5. The output is taken from the collector of Q4 and is a current, not a voltage. Thus Kitty Hawk is a current output amplifier, also known as a transconductance amplifier.

Ultra low capacitance diode D5 is applied as an anti-saturation clamp, but this may be unnecessary since the output power transistors will almost certainly go into clipping at far smaller signal swings than the giant swings necessary to saturate Q4.

Kitty Hawk's supply is passively filtered by R1-C2 and then actively regulated by two LM317L voltage regulator chips (in the cute TO-92 transistor packages) connected in series. Supply is regulated, and that regulated supply is regulated again. Zener diode D3 guarantees that U1's input-to-output voltage always remains comfortably below the datasheet Absolute Maximum rating (30 volts).

Component footprints C6, R9, R10 are provided for the convenience of the builder, to allow experimentation with other choices of voltage gain.

REV.B 28 DEC 2021

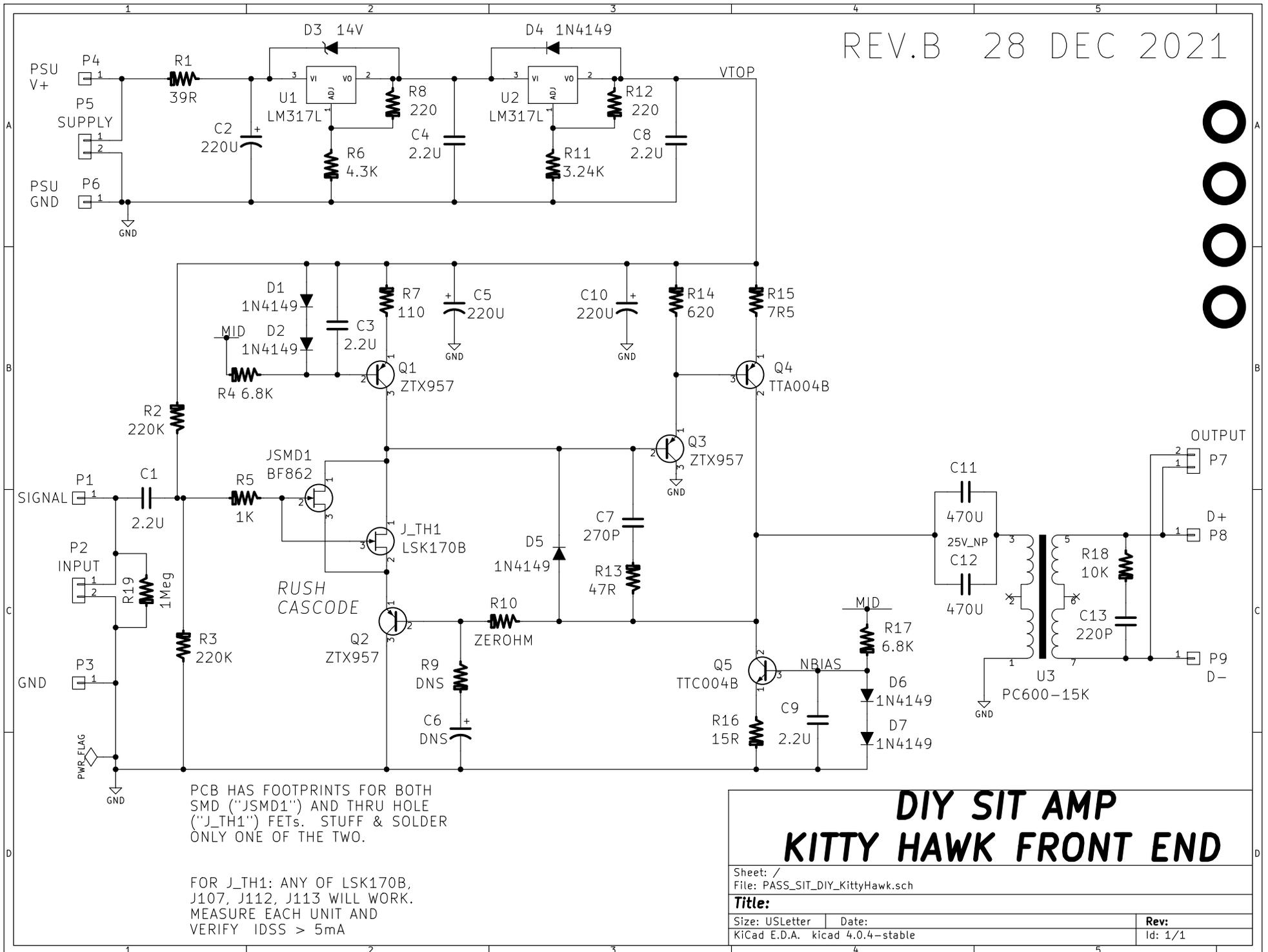

DIY SIT AMP KITTY HAWK FRONT END

Sheet: /		File: PASS_SIT_DIY_KittyHawk.sch	
Title:			
Size: USLetter	Date:	Rev:	
KiCad E.D.A. kicad 4.0.4-stable		Id: 1/1	

Lexington Front End

Lexington, like its British warship predecessors Marauder and Dreadnought, has no Edcor step-up transformer. Instead it has an onboard DC-to-DC converter called JBOOST2 (third schematic sheet) which provides a supply named POS_BOOSTED, in the neighborhood of 55-60 volts. The circuit technology of JBOOST2 is different from JBOOST1 used previously; now it's an isolated DC-to-DC converter module, manufactured by CUI Inc. 24V DC input, isolated 24V DC output.


Zener diode D4 drops the ~34 volt supply down to 23 volts, within the spec range of U8. The isolated 23 volt output, presented between pins 4 and 6, is added to the 34 volt input, creating an output between node CAROL and ground, of about 57 volts. This is passively filtered by L2-C18 and run through a darlington capacitance multiplier for additional smoothing. D7 gives over voltage protection and R34 is a bleeder.

Front Ends with an Edcor transformer can invert their output phase via the simple trick of swapping the transformer output leads. Lexington, having no transformer, resorts to opamps and a switch, as shown on the second schematic page.

Lexington's signal path includes an input differential pair of NPNs (Q2, Q4) with resistor loads (R13, R16).^{*} These differential signals are applied to the emitters of a pair of PNPs (Q5, Q8) operating in common base mode. They drive an NPN current mirror (Q6, Q7). Overall, this topology is called a Folded Cascode, and it functions as a single amplifying stage whose gain is simply the gm of the input pair with degeneration.

The mirror output drives the (grounded) frequency compensation capacitor C9, thus Lexington uses simple lag compensation (not the more common Miller compensation). Hefty emitter follower Q10, in a TO-220 power transistor package, drives the Front End output. Q10 is loaded by constant current source Q9, also a TO-220 device.

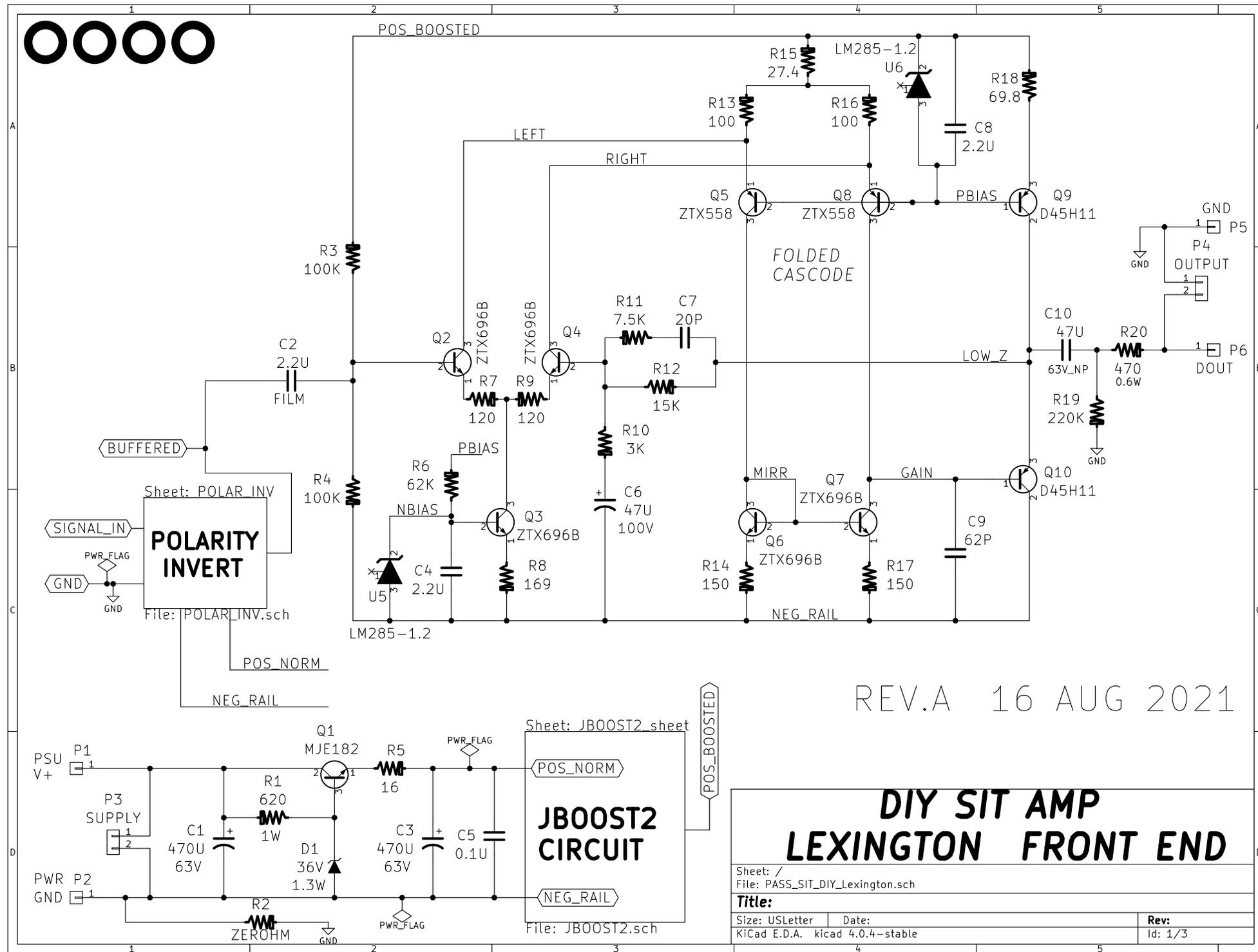^{*}what about R15?? It is merely a level shifter. The current in R15 is constant, therefore the voltage across R15 is also constant.



REV.A 16 AUG 2021

DIY SIT AMP LEXINGTON FRONT END


Sheet: /
File: PASS_SIT_DIY_Lexington.sch

Title:

Size: USLetter Date:
KiCad E.D.A. kicad 4.0.4-stable

Rev:
Id: 1/3

REV.A 16 AUG 2021

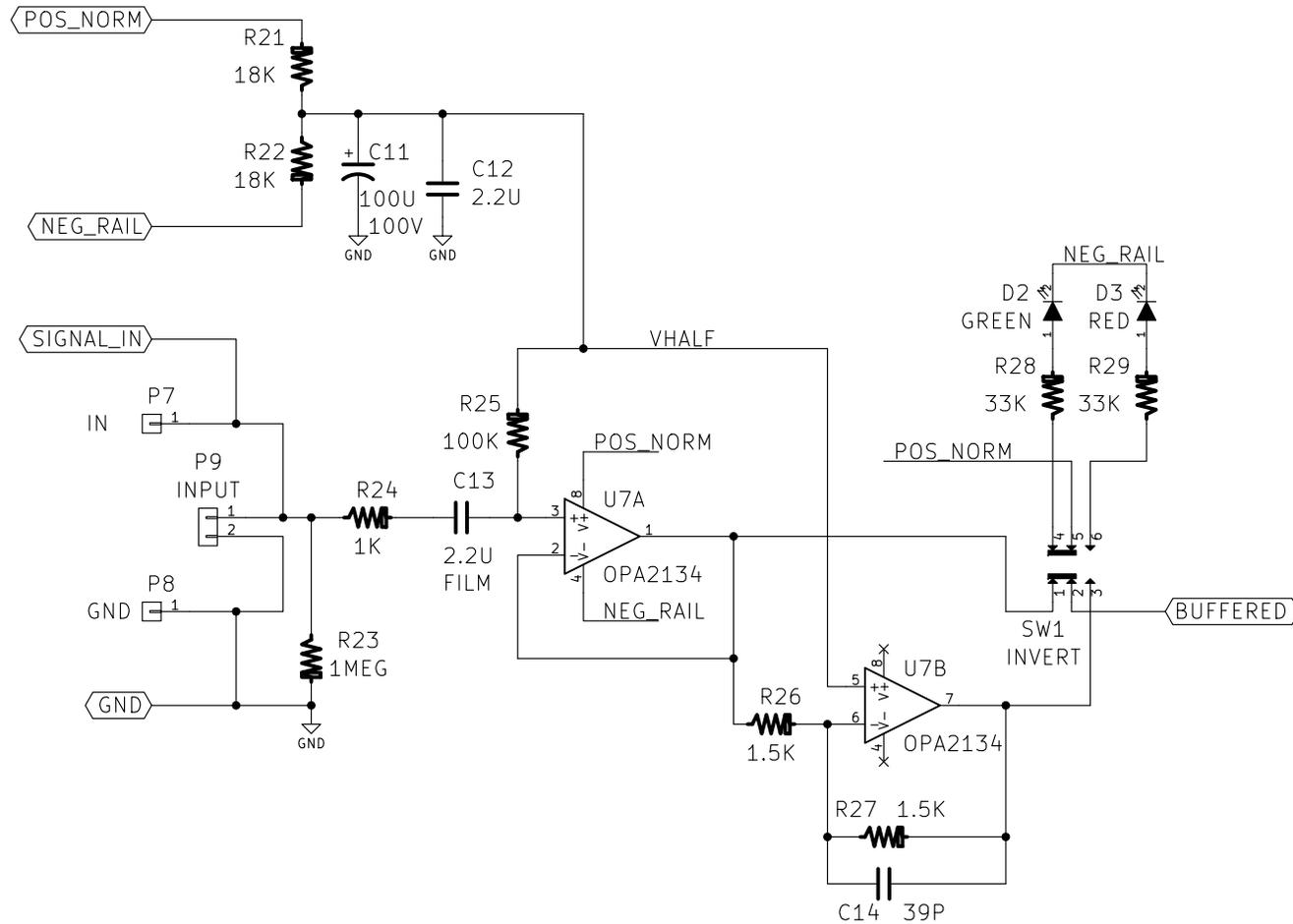

POLARITY INVERT

Sheet: /POLAR_INV/
File: POLAR_INV.sch

Title:


Size: USLetter Date:
KiCad E.D.A. kicad 4.0.4-stable

Rev:
Id: 2/3

Ferrite beads are
Laird 28C0236-0EW-10
998 ohms @ 100 MHz
5 Amps 10 mOhm

Inductors are Bourns
RL622-100K-RC
3 Amps; 45 mOhm

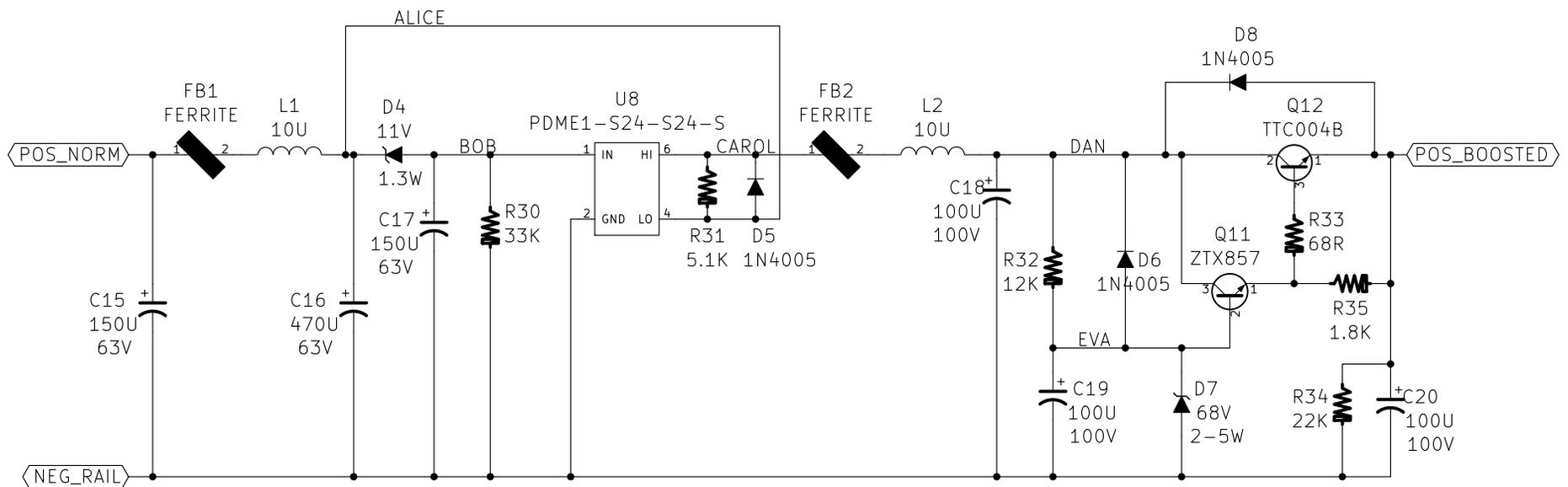Electrolytic caps are
Panasonic EEU-FR
or EEU-FM



REV.A 16 AUG 2021

JBOOST2

Sheet: /JBOOST2_sheet/
File: JBOOST2.sch

Title:

Size: A Date:
KiCad E.D.A. kicad 4.0.4-stable

Rev:
Id: 3/3

Hornet Front End

When DigiKey and Mouser each reported stocking more than fifty thousand pieces of NJFETs and PJFETs in thru hole packages, it suddenly became practical to create a Front End which put them to use. In particular, the complementary source follower pair *without degeneration resistors* is now a viable and pragmatic option for an output stage.

Additionally, since the J175 (Pch) and J111 (Nch) are both relatively high gm devices, they can be used as cascodes for constant current sources. A CCS built this way is simple (3 components), works well at high frequencies (the JFET shields the LM334 from HF signals), and eats relatively little headroom (thanks to the small Vgs requirements of a high gm device).

Putting this all together, we get a Front End loaded with cascodes. The supply filters/regulators are connected in cascode. The first gain stage's CCS load (Q3-U1) is a cascode. The second gain stage's CCS load (Q7-U2) is a cascode. And the input circuit itself (Q4-R9-Q2) is a Rush Cascode with degeneration. There's a whole lotta cascodin' goin' on.

The voltage between the output transistors' gates is V(CAROL) minus V(DAVE), and it appears across trimmer resistor R1. Since the current flowing in R1 is constant {set by U2}, changing the resistance of R1 changes the voltage dropped from CAROL to DAVE. This changes the Vgs's of the output transistors, and sets their Class A bias current.

Setting the output stage bias current is, therefore, simple. We merely clip our millivoltmeter's crocodile clips onto the legs of resistor R17 and monitor its voltage. From Ohm's Law, $\text{Current} = \text{Voltage} / \text{Resistance}$ and we know both Voltage (it's the millivoltmeter reading) and Resistance (20 ohms). Voila! Just twirl the shaft of RV1 until the voltage across R17 is 480 millivolts and stop. $\text{Current} = 480\text{mV} / 20\text{ohms} = 24 \text{ milliamps}$. Done!

Beware, these devices heat up quickly during IDSS measurement. Use a pushbutton and measure IDSS in the first half second after powering.

Pequod Front End

Pequod has only one objective: to deliver a simple Front End whose components are easy to source, inexpensive to buy, and straightforward to build. Make it easy for someone who already owns New-Old-Stock VFET devices, but has no PCBs at all, to put together a Ship Of Theseus amplifier inexpensively.

Pequod is merely an opamp follower driving an Edcor transformer, plus the AC coupling capacitors necessary for single ended supply operation. And that's all.

A couple of extras have been added, which increase flexibility without dramatically increasing cost or complexity. For example, there are two DIP-8 sockets on the PCB. One of them accepts single opamp chips like the LT1122, and the other socket accepts dual opamp chips like the OPA1656. This gives builders the flexibility to experiment with whichever opamp types they please.

The sockets are spaced far apart and away from other components, making it easier to fit discrete opamp modules like the products from Sparkos, Burson, etc. For even more experimentation.

Zener diode ZD1 drops the opamp supply below 26V, to accommodate chips that can work on 30V but not 36V supply.

Output load resistor R7 increases the bias current flowing in the opamp's output stage at all times, leading to reduced crossover distortion in many cases.

