



FIGURE 8: The complete DC 100 driver circuit. The output stage is the same as in the Servo 100.