

Take advantage of current-feedback amps for high-frequency gain

Barry Harvey, Elantec Inc


Current-feedback amplifiers have virtues unavailable in the traditional voltage-feedback design. To take full advantage of these virtues, you'll need to know the strengths and weaknesses of current-feedback amplifiers and techniques for coping with amplifier problems.

Current-feedback amplifiers develop high-frequency gain in a manner that is fundamentally different from that of voltage-feedback amplifiers. These amplifiers are not just input stages, but full-fledged amplifier circuits that have some outstanding characteristics: very high slew rates, -3-dB bandwidths almost constant with increasing circuit gain, and low high-frequency distortion. Almost all commercial current-feedback amplifiers offer these benefits, but many exhibit such seldom publicized limitations as slew distortion, thermal settling errors, and so-so gain accuracy.

Fig 1 illustrates the simplest current-feedback-amplifier circuit. Transistors Q₁ through Q₄ form a complementary buffer, so the - INPUT terminal is actually an output—a buffered replica of the voltage at the + INPUT. Q₃ and Q₄ idle at a quiescent current proportional to the geometric mean of i₁ and i₂ and a scale factor dependent on the relative sizes of Q₁ through Q₄. When the feedback loop is at null, no error current flows to the - INPUT, and Q₃ and Q₄ draw equal collector currents (ignoring base-current errors). Q₈ and Q₉ mirror Q₃'s collector current and transfer the value to the gain node. Q₅ and Q₆ mirror Q₄'s collector current and use the current to balance the Q₈-Q₉ current mirror at the gain node. Transistors Q₁₁ through Q₁₄ provide buffering between the gain node and the output terminal.

To understand the behavior of the circuit, assume that the + INPUT and output terminals are resting at

0V. If you apply a 1V positive step to the + INPUT, the Q₁-through-Q₄ input buffer quickly replicates the step at the - INPUT terminal. Because the output terminal has not had time to react, the step voltage is impressed across feedback resistor R_F. Assuming a value of 1 kΩ for R_F (typical in most cases), the 1V step causes a 1-mA transient current to flow through R_F. This current flow increases Q₃'s current by 500 μA and decreases Q₄'s current by 500 μA. If both current mirrors have a gain of 1, Q₉'s collector current will increase by 500 μA, and Q₆'s collector current will decrease by

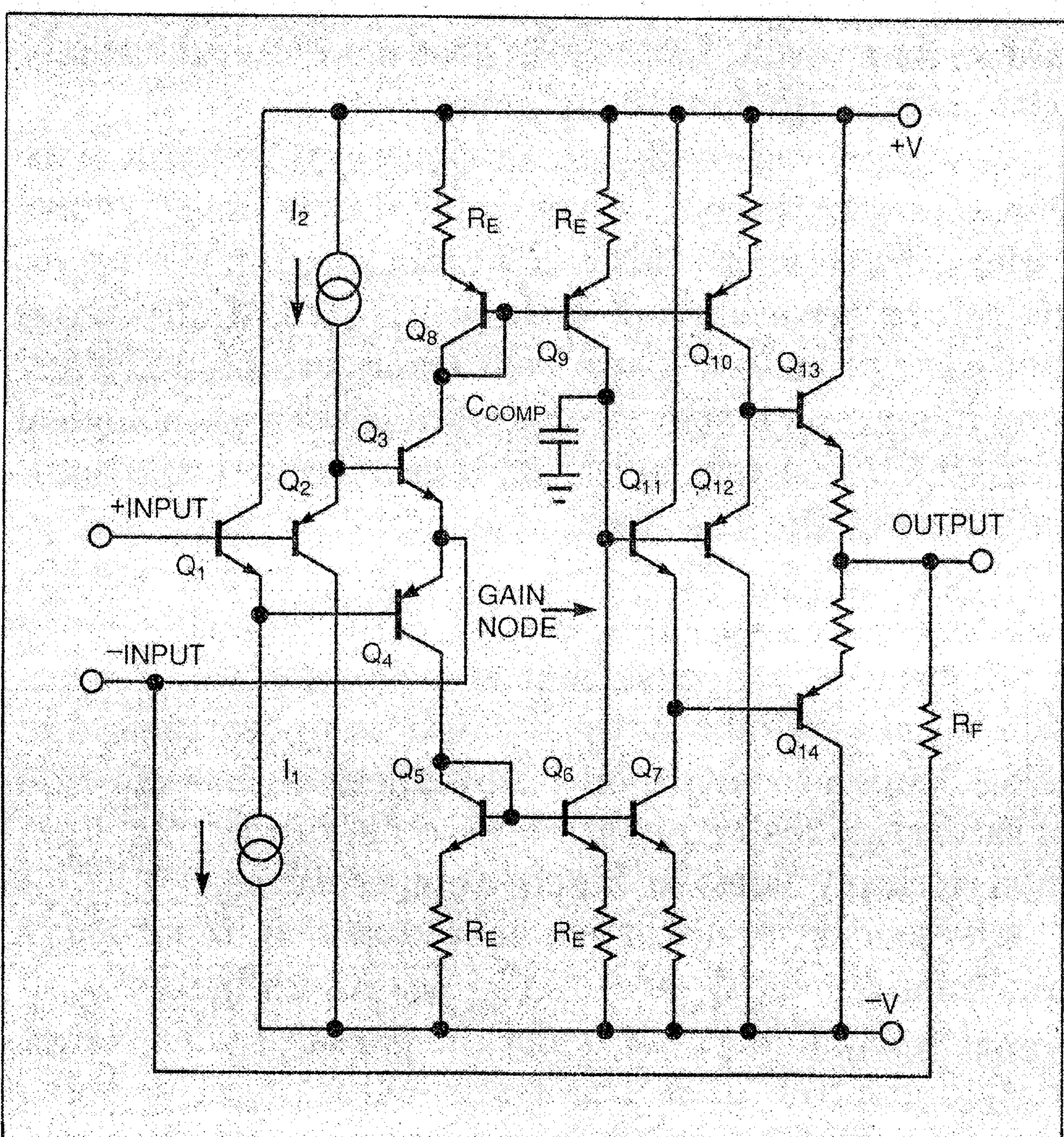

CURRENT-FEEDBACK AMPLIFIERS

500 μA. The 1-mA transient-error current through R_F arrives at the amplifier's gain node and slews the node positive at a rate determined by the R_F-C_{COMP} time constant. The amp's output follows the gain node, moving in a positive direction until the circuit reaches equilibrium. At this point, almost no current flows through R_F and currents to the gain node balance.