



$$\text{NEGATIVE FEEDBACK} \Rightarrow V_{\text{err}} = 0 \Rightarrow V_{\text{in}} = V_{R3} \quad (1)$$

$$\text{HIGH-IMPEDANCE OF AMPLIFIER INPUTS} \Rightarrow i_{R2} = i_{R3} \quad (2)$$

$$\Rightarrow \frac{V_{R3}}{R_3} = \frac{V_{R2}}{R_2} \quad (3)$$

$$V_{\text{out}} = V_{R2} + V_{R3} \quad (4)$$

$$\text{SUB } (3) \text{ INTO } (4) \Rightarrow V_{\text{out}} = V_{R3} \frac{R_2}{R_3} + V_{R3} \quad (5)$$

$$\text{SUB } (1) \text{ INTO } (5) \Rightarrow V_{\text{out}} = V_{\text{in}} \left(1 + \frac{R_2}{R_3} \right) \quad (6)$$

$$V_{\text{LS}} + V_{R4} = V_{\text{out}} \quad (7)$$

$$\text{SUB } (6) \text{ INTO } (7) \Rightarrow V_{\text{LS}} = V_{\text{in}} \left(1 + \frac{R_2}{R_3} \right) - V_{R4}$$

THE THING WE
WANT TO BE AN
EXACT, NON-DISTORTED MULTIPLE
OF THE INPUT SIGNAL

AN EXACT, NON
DISTORTED MULTIPLE
OF THE INPUT SIGNAL

AN ERROR VOLTAGE OUTSIDE
THE FEEDBACK LOOP