

Class-D LC Filter Designer

1 Class-D Configuration

Select the output configuration on the right.

Filter Type

Output Configuration

Load Factor

Enter the speaker load, desired cutoff frequency, and quality factor.

Speaker Load (R_{Load}) Ω

Cutoff Frequency kHz

Quality Factor (Q)

2 Calculated Components

The calculated LC filter component values are shown below.

Inductor (L) μH

Capacitor (C_g) μF

Capacitor (C_{BTL})

Total Cap SE Equivalent μF

3 Graph & Verify

Enter standard inductor and capacitor values below to graph & verify.

Inductor (L) μH

Capacitor (C_g) μF


Capacitor (C_{BTL})

Total Cap SE Equivalent μF


Cut-Off Frequency kHz

Quality Factor (Q)


Single-Ended (SE) - AD or BD

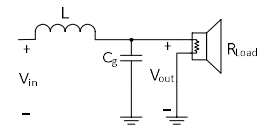


BTL - Differential - AD Mode

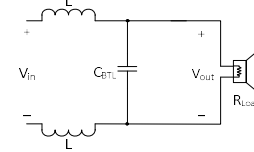

BTL - Common Mode - BD or AD Mode

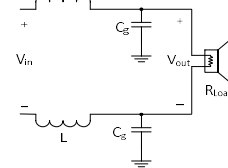


BTL - Hybrid - AD Mode

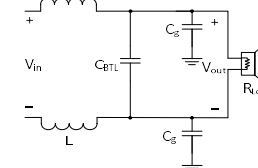


Transfer Function

$$\frac{1}{1 + s \cdot \frac{L}{R_{Load}} + L \cdot C \cdot s^2}$$

Gain vs Frequency

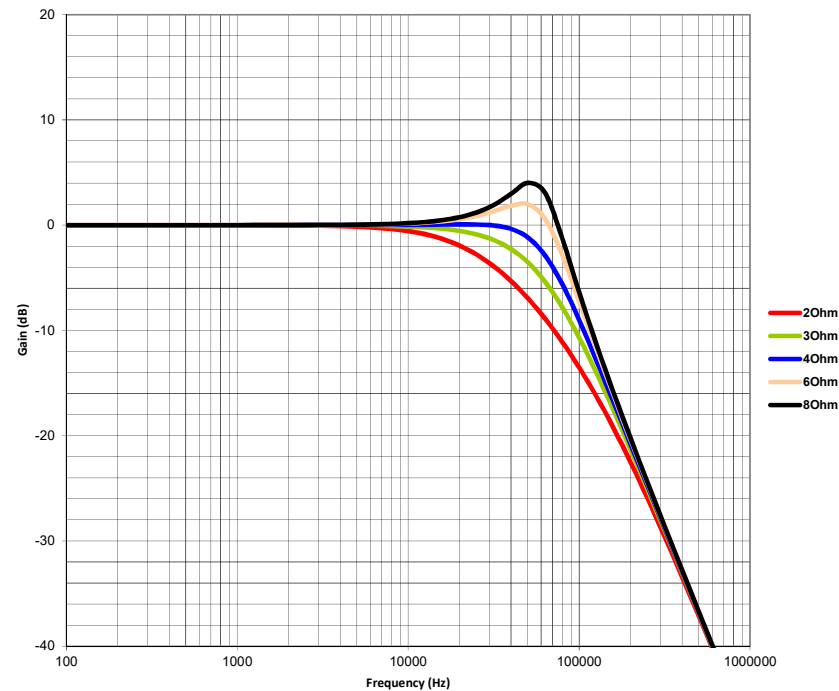

Zoom (Gain vs Frequency)

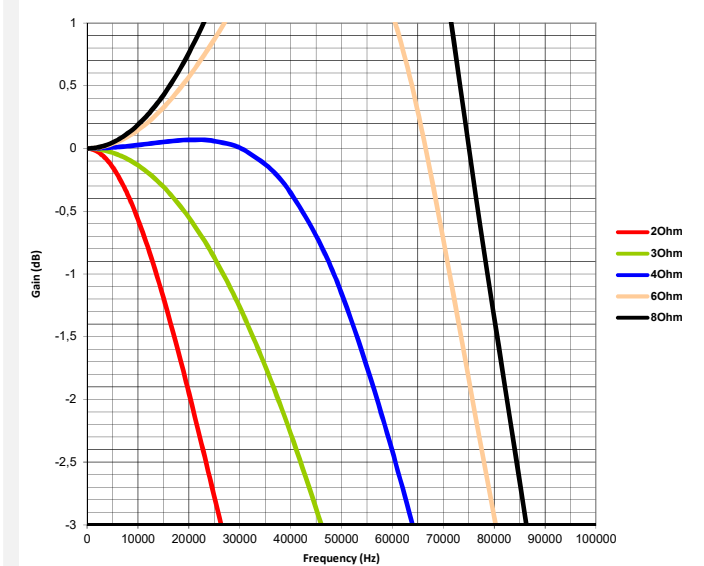

Graph Settings

Enter up to 5 different loads to graph.

		Q	
Load 1	2	Ω	0,378
Load 2	3	Ω	0,567
Load 3	4	Ω	0,756
Load 4	6	Ω	1,134
Load 5	8	Ω	1,512