



- This is a concept design. It is not debugged or optimized
- Very simple (6 active devices) 50W amplifier. No electrolytics in the feedback loop



- Classic CFA response – high SR and very wide bandwidth