

## Class-D LC Filter Designer

### 1 Class-D Configuration

Select the output configuration on the right.

Filter Type

Output Configuration

Load Factor

Enter the speaker load, desired cutoff frequency, and quality factor.

Speaker Load ( $R_{Load}$ )   $\Omega$

Cutoff Frequency  kHz

Quality Factor (Q)

### 2 Calculated Components

The calculated LC filter component values are shown below.

Inductor (L)   $\mu H$

Capacitor ( $C_g$ )   $\mu F$

Capacitor ( $C_{BTL}$ )

Total Cap SE Equivalent   $\mu F$

### 3 Graph & Verify

Enter standard inductor and capacitor values below to graph & verify.

Inductor (L)   $\mu H$

Capacitor ( $C_g$ )   $\mu F$


Capacitor ( $C_{BTL}$ )

Total Cap SE Equivalent   $\mu F$


Cut-Off Frequency  kHz

Quality Factor (Q)


Single-Ended (SE) - AD or BD

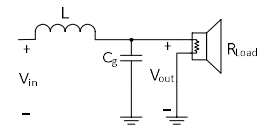


BTL - Differential - AD Mode

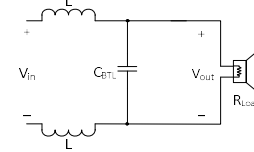

BTL - Common Mode - BD or AD Mode

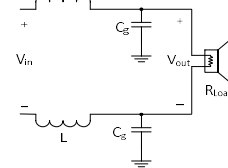


BTL - Hybrid - AD Mode

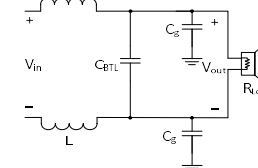


Transfer Function

$$\frac{1}{1 + s \cdot \frac{L}{R_{Load}} + L \cdot C \cdot s^2}$$

Gain vs Frequency

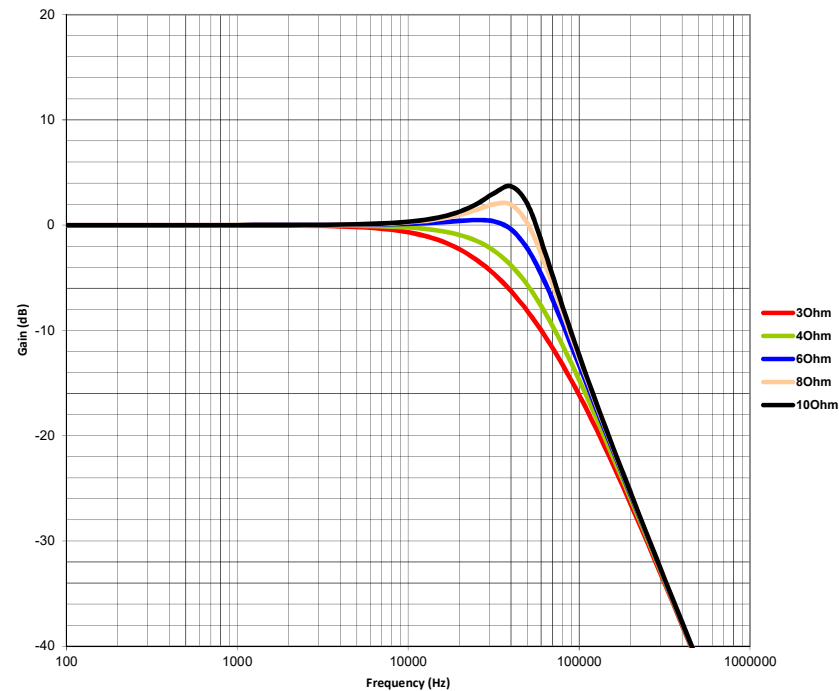

Zoom (Gain vs Frequency)

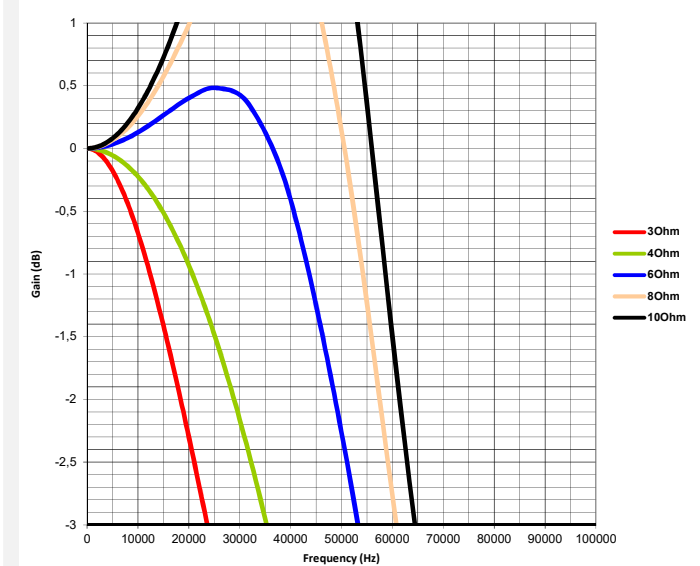

#### Graph Settings

Enter up to 5 different loads to graph.

Load 1	3	$\Omega$
Load 2	4	$\Omega$
Load 3	6	$\Omega$
Load 4	8	$\Omega$
Load 5	10	$\Omega$

Q
0,430
0,574
0,860
1,147
1,434